

MID TERM EXAMINATIONS – April 2024

Programme	: B.Tech.	Semester	: Winter 2023-24
Course Title/ Course Code	: Electric Circuits and Systems / EEE1001	Slot	: A21+A22+A23
Time	: 1 ½ hours	Max. Marks	: 50

Answer all the Questions

Q.No.	Sub. Sec.	Question Description	Marks
1		Find the drop between terminals 'm' and 'a' in the network shown in Fig. 1. Also find out the power dissipation through those three 5 Ω (ohm) resistances.	10

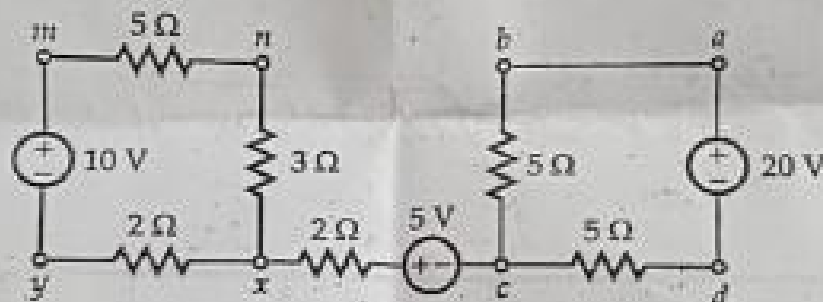


Fig.1

- 2 What resistance should be connected across x-y in the circuit shown in Fig.3 such that maximum power is developed across this load resistance? What is the amount of this maximum power?

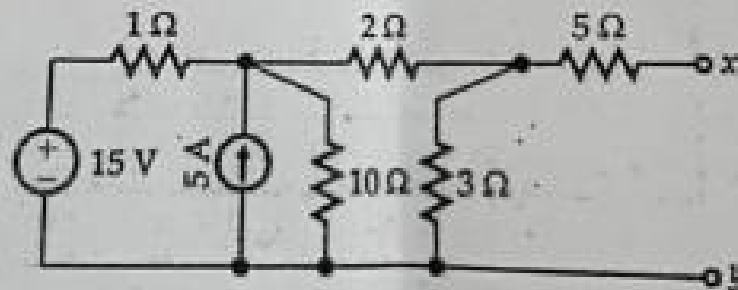


Fig.3

- 3 (a) An impedance of $10\angle 37^\circ \Omega$ (ohm) is in parallel with another impedance $18\angle 56.3^\circ \Omega$ (ohm) and a voltage of $250\angle 0^\circ$ V is applied across the combination.

Find the source current and show the phasor diagram of the currents with respect to the applied voltage.

4

Consider a linear time inverse continuous system given by

$$\frac{d^2 y(t)}{dt^2} - 9 \frac{dy(t)}{dt} + 14y(t) = \frac{dx(t)}{dt} + 2x(t) \text{ the input is } x(t) = e^{-3t} u(t).$$

Find, (i) Natural response

(ii) Forced response.

(iii) Total response.

for initial condition

$$y(0^+) = 9, \frac{dy(0^+)}{dt} = 0$$

5

Find V_2 in the circuit of Fig. 4 such that current in the left hand loop is zero. Assume $V_1 = 25 \angle 0^\circ \text{ V}$

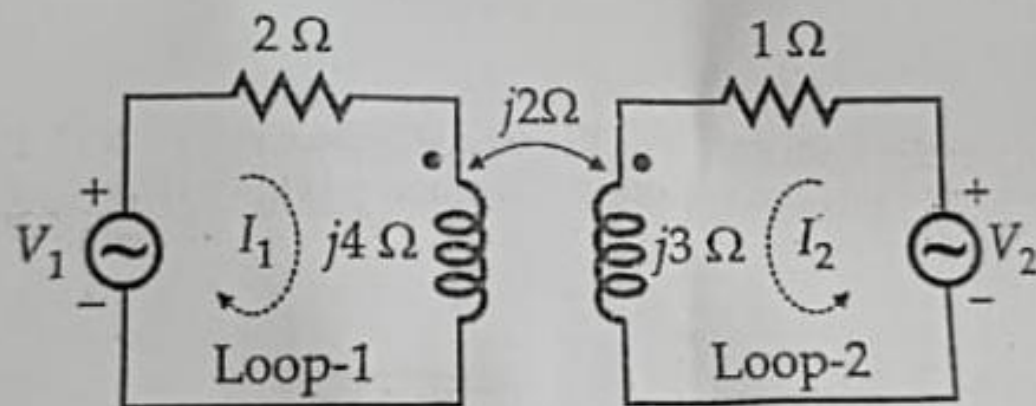


Fig.4

