



MID TERM EXAMINATIONS – October-November 2023

Programme	: B.Tech.	Semester	: Fall 2023-24
Course Title/ Course Code	: Electric Circuits and Systems / EEE1001	Slot	: B11+B12+B13
Time	: 1 ½ hours	Max. Marks	: 50

Answer all the Questions

Q.No. Sub.
Sec.


Question Description

Marks

Design the DC circuit by using minimum 29 (series and parallel combination) resistors and 1 DC source. The circuit must have 4 delta-star and 1 star-delta transformation. Calculate the equivalent resistance and total current? Assume the DC voltage and resistance values.

10

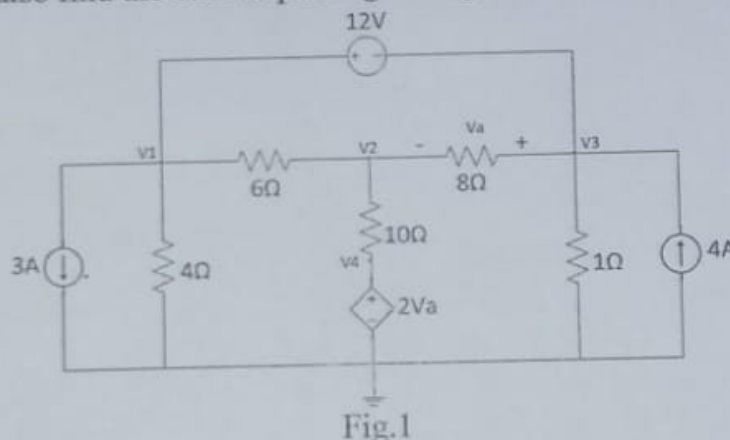- 2 (a) Solve the given network circuit shown in Fig.1 by using Nodal analysis after adding 5 Ω resistor in series with the 12V supply. Find out node and branch voltages V_1 , V_2 , V_3 and V_4 and also find the current passing through 10 Ω resistor branch?



5

- (b) Explain superposition theorem with one suitable numerical (3 sources)?

5

Extract the natural, forced and total response in the second order equation.

The input is $x = e^{-2t} \times u(t)$

Conditions: $y(0)=3$, $\frac{dy}{dt}(0)=4$ for the natural response. Assume the second order equation and other missing data.

10

Draw magnetic circuit by using minimum 18 (series and parallel combination) inductors. Calculate the equivalent inductance? Assume the all inductance, dot convention and mutual inductance values.

10

Crystal diodes having an internal resistance of 20 Ω . If the applied voltage is $50\sin\omega t$ and the load resistance is 800 Ω . Find the maximum current, dc current, rms current, ac power input, dc power output, dc output voltage and efficiency?

10



$$V = V_0 \sin \omega t$$